



Bu-Ali Sina University
Department of Computer Engineering
Synthesis of Digital Systems (SDS2022)

Homework Solution #2

Neda Motamediraad
(40113224005)

Homework and Project Solutions
<https://github.com/nedaraad/MSc-Synthesis.git>

Q.1 States Reduction of FSM

Given is Machine M

- Find the minimal machine (in the number of states) that is equivalent to machine M
- Draw the triangular table of machine M
- Solve the triangular table
- Find the maximal compatible groups of states.
- Solve graphically the covering/closure problem.
- Formulate algebraically the binate covering problem.
- Realize the machine using JK flipflops and combinational gates.

a	d/-	f/0
b	c/1	h/0
c	d/0	h/0
d	c/0	a/0
e	-/-	f/0
f	e/0	a/0
g	c/1	-/-
h	b/1	a/1


Machine M

Q1. Solution

**Implication Table
(Triangular Table)**

b	cd fh						
c	fh	X					
d	cd fh	X	ah				
e	✓	fh	fh	af			
f	de	X	de ah	cd	af		
g	cd	✓	X	X	✓	X	
h	X	X	X	X	X	X	bc

Compatibility Classes		Incompatibility Classes	
g	—	g	(gh)
f	• —	f	(fg) (fh) (gh)
e	(ef) (eg)	e	(ef) (fgh)
d	(de) (ef) (eg)	⋮	⋮
c	(de) (ef) (eg)	d	(dfgh) (eh)
b	(bg) (de) (ef) (eg)	⋮	⋮
a	(ae) (af) (bg) (de) (ef) (rg)	c	(cdfgh) (ceh)
a	(aef) (bg) (de) (eg)	⋮	⋮
		b	(bcdfh) (bceh) (cdfgh)
		⋮	⋮
		a	(acdgh) (abcdh) (bcdfh) (bceh)

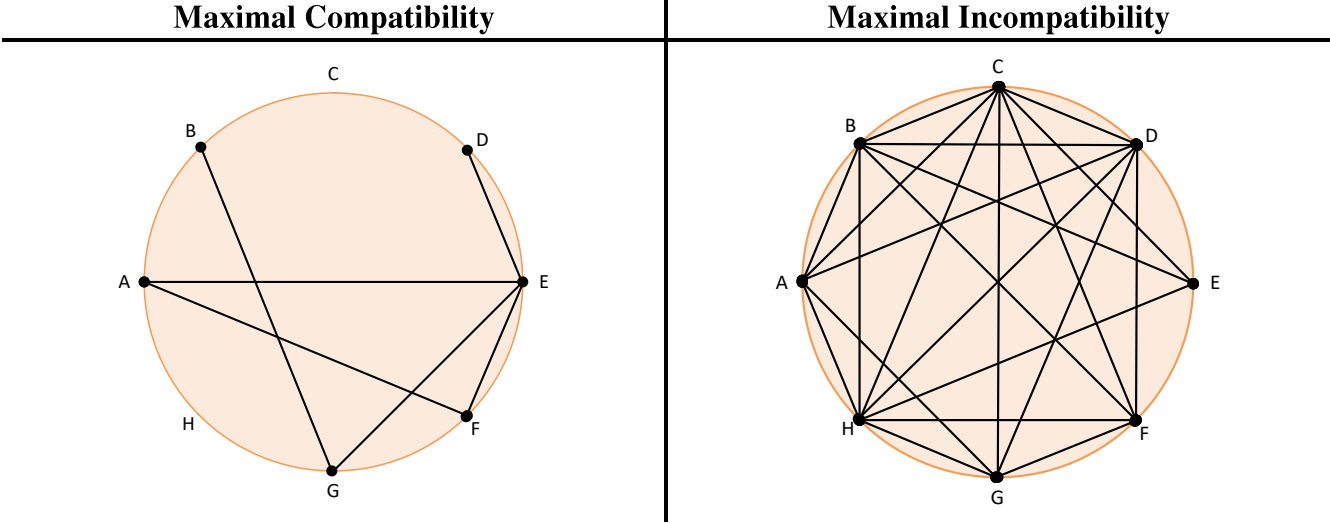

Closure Table and Equations			
		0	1
$A \leftarrow$	aef	de/0	af/0
$B \leftarrow$	bg	c/1	h/0
$C \leftarrow$	de	c/0	af/0
	eg	c/1	f/0
$D \leftarrow$	c	d/0	h/0
$E \leftarrow$	h	b/1	a/1

$$U = \min \{NSMC, NSOC\}$$

$$U = \min \{6, 8\} = 6$$

$$L = \max \{NSMI_1, NSMI_2, \dots, NSMI_i\}$$

$$L = \max \{5, 5, 5, 4, 5\} = 5$$

$$L \leq K \leq U \rightarrow 5 \leq K \leq 6 \rightarrow K = 5 \checkmark$$

$$K = 5$$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	1	1		
	01	0	0		
	11				
	10				

$J_1 = \bar{X}$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	1			
	01	0			
	11				1
	10				1

$J_2 = \bar{X} + Q_3$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	0	1	1	
	01	0	0	0	
	11				
	10				

$J_3 = \bar{X} \cdot Q_2$

		Q_1Q_2			
		00	01	11	10
Q_3X	00			0	
	01			1	
	11			1	1
	10				

$K_1 = X$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	0		1	
	01		1	1	
	11			0	
	10			1	

$K_2 = X \cdot \bar{Q}_3 + \bar{X} \cdot Q_1$

		Q_1Q_2			
		00	01	11	10
Q_3X	00				
	01				
	11			1	1
	10			0	1

$K_3 = Q_2 + X$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	1	1	1	
	01	0	0	0	
	11			0	0
	10			1	1

$D_1 = \bar{X}$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	1	1	0	
	01	0	0	0	
	11			1	1
	10			0	1

$D_2 = \bar{X} \cdot (\bar{Q}_1 \cdot Q_2) + X \cdot Q_3$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	0	1	1	
	01	0	0	0	
	11			0	0
	10			1	0

$D_3 = \bar{X} \cdot Q_2$

		Q_1Q_2			
		00	01	11	10
Q_3X	00	1	1	1	
	01	0	0	0	
	11			0	0
	10			1	1

$$Z = \bar{Q}_1 \cdot Q_2 + \bar{X} \cdot Q_2 \cdot Q_3$$


$$Z = Q_2 \cdot (\bar{Q}_1 + \bar{X} \cdot Q_3)$$

$$D_2 = \bar{X} \cdot \bar{Q}_1 + X \cdot Q_3 + \bar{X} \cdot \bar{Q}_2$$

$$D_2 = \bar{X} \cdot (\bar{Q}_1 + \bar{Q}_2) + X \cdot Q_3$$

$$D_2 = \bar{X} \cdot (\bar{Q}_1 \cdot Q_2) + X \cdot Q_3$$

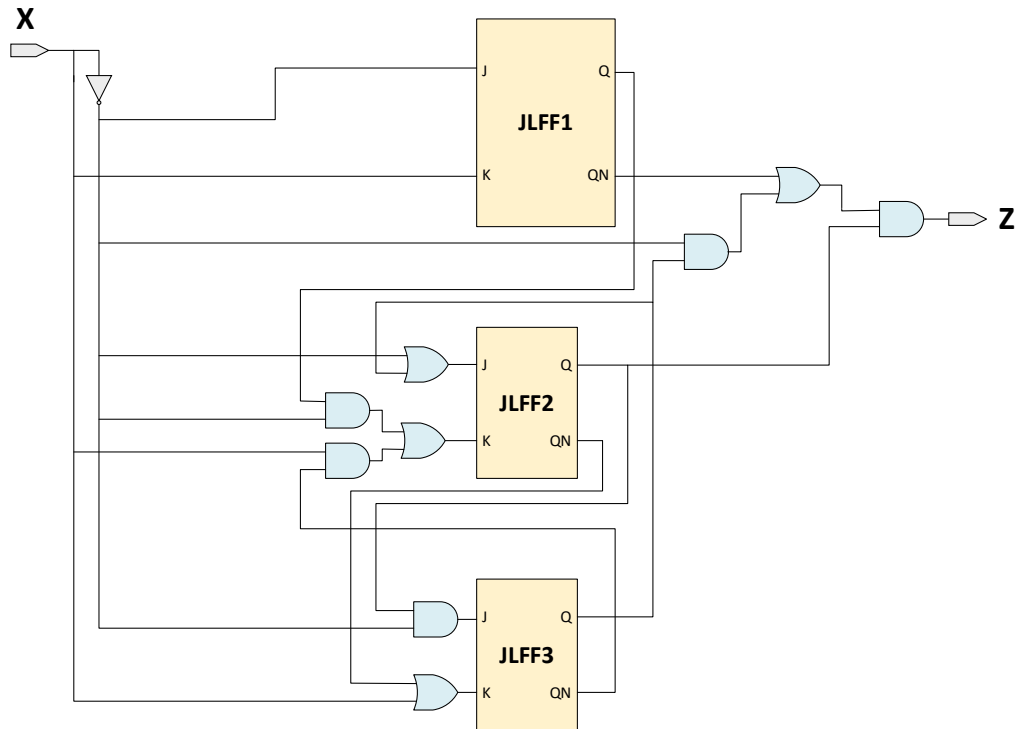Realize the machine using JKFF and Logic Gates



Realize the machine using DFF and Logic Gates

